

This voltage divider will turn on the transistor if there is enough light shining on the photo-resistor. If the transistor is ON, the other section of this circuit will be activated, since it can then be connected to the circuit's 'ground.'

The three parallel branches: "drain", "light", "delay" are the core of how this circuit works. They each provide a different resistance, and thus have different electric current supplied at the instant the transistor turns on. The interplay between these three branches is complex, and drives this analog circuit's operation.

Since this circuit is NOT consistent in its operation over time, let's consider what happens in order when the transistor is first turned on:

First, the 'delay' branch has no resistor, so it takes on the vast majority of the newly-supplied current. This starts to charge the capacitor: quickly at first, then slower.

Second, as the capacitor fills, it builds up a voltage across its two plates. When that voltage equals the 'forward voltage' of the LED, a critical change happens:

The LED (and whole light branch) can turn ON when there is enough built-up voltage on the capacitor. Although it is dim at first, it quickly brightens as the capacitor charges asymptotically to its max.

While this whole parallel subcircuit is active, the 'drain' branch has too high of a resistance (compared to the other two branches) to be more than a leakage current. In the active state, you can basically ignore the 'drain' branch since it carries so very little current.

When the circuit is no longer active (the transistor turns off), the 'drain' branch has its useful moment. This resistor provides a path for the capacitor to slowly drain its built-up voltage, so that it can reset itself automatically to be ready for the next time this sub-circuit is activated by the transistor.

2015 Mission Possible Ohio State Champions

**Mason High School Applied Technology**

Sheet: /scioly-delayed-light/

File: scioly-delayed-light.kicad\_sch







**Title: Science Olympiad Real-Life RC Circuit**

Size: USLetter Date: 2025-03-20

KiCad E.D.A. 8.0.6

**Rev: v1.0**

Id: 2/9

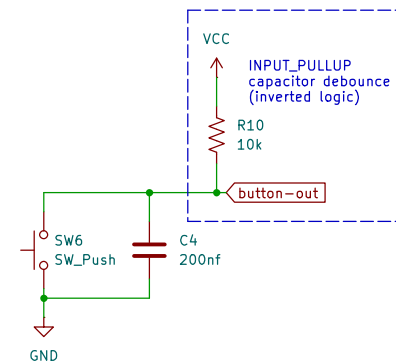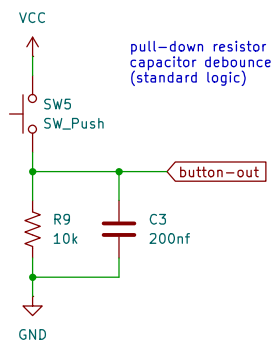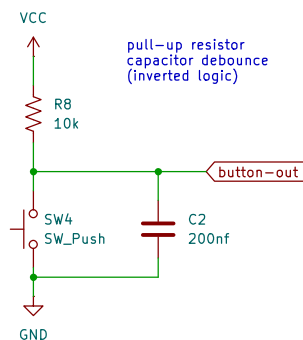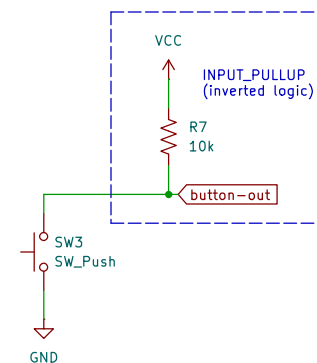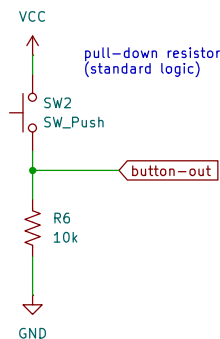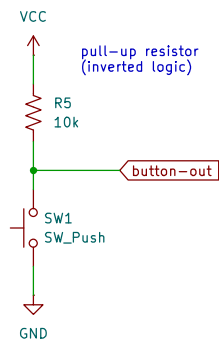

`Floating Pin` – without a pull-up or pull-down the value of the button can change erratically when the button is disconnected

`Standard Logic` – HIGH when pressed, LOW when un-pressed

`Inverted Logic` – LOW when pressed, HIGH when un-pressed

`Capacitor Debouce` – a capacitor will take time to charge, effectively applying a physical debounce: 100nF to 1 $\mu$ F common

6 common ways to use buttons with microcontrollers

**Mason High School Applied Technology**

Sheet: /momentary-button/

File: momentary-button.kicad\_sch


**Title: Button Implementation Strategies**

Size: USLetter Date: 2025-03-20

KiCad E.D.A. 8.0.6

**Rev: v1.0**

Id: 3/9

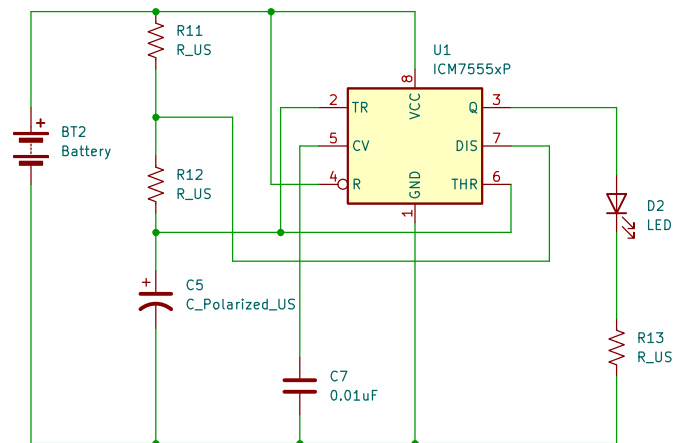

A classic design that lets an LED turn on and off.

**Mason High School Applied Technology**

Sheet: /555-basic-blinker/

File: 555-basic-blinker\_sch.kicad\_sch

**Title: 555 Basic Blinker**


Size: USLetter

Date:

**Rev: v1.0**

KiCad E.D.A. 8.0.6

Id: 4/9

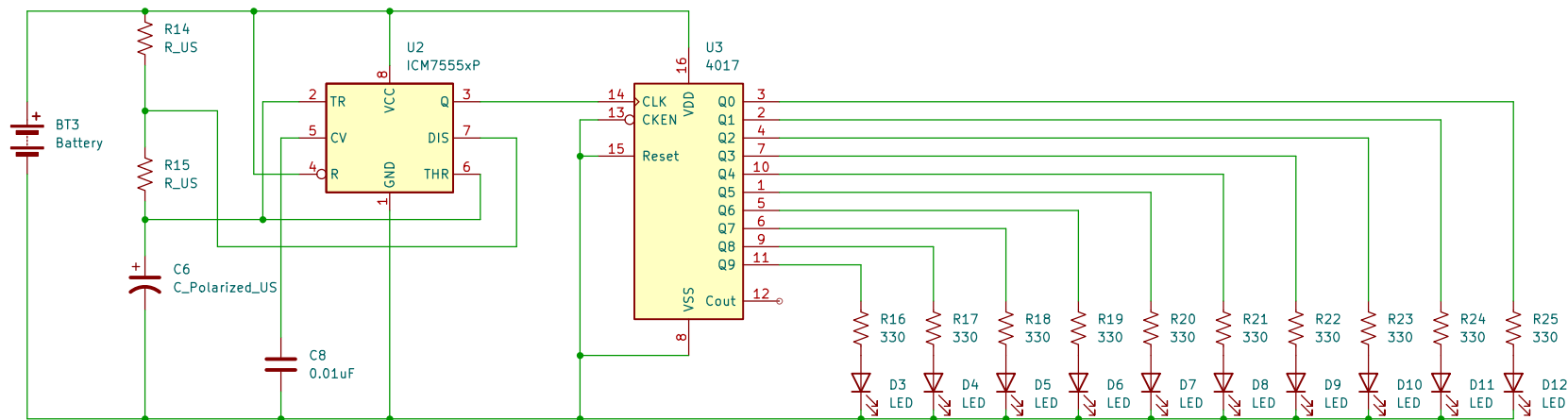

Video explainer: <https://youtu.be/WdhzOjQjNrg>  
 "Learn Electronics | LED chaser with 555 & 4017"  
 — TheElectroBench, YouTube

Using a decade counter to setup some chasing lights

**Mason High School Applied Technology**

Sheet: /night-rider/

File: night-rider.kicad\_sch

**Title: Night Rider (LED Chaser)**

Size: USLetter


Date:

**Rev: v1.0**


KiCad E.D.A. 8.0.6

Id: 5/9

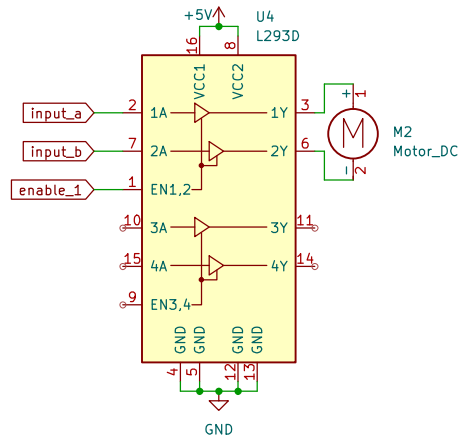
H-Bridge motor driver  
"Forward" "Reverse" "Stop" "OFF"



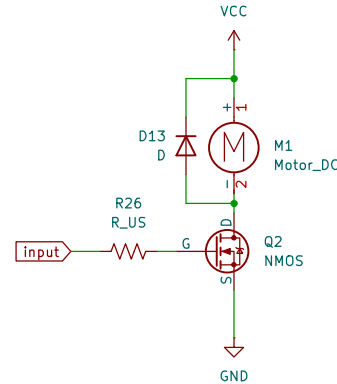
Single MOSFET control  
DC brushed motor only  
Only 'Forward' or OFF



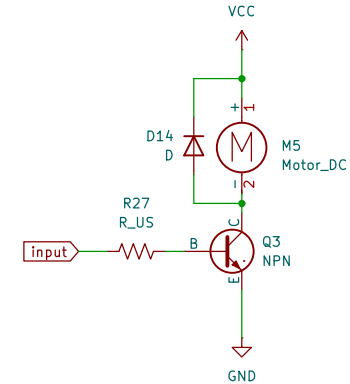
Single BJT Transistor control  
DC brushed motor only  
Only 'Forward' or OFF



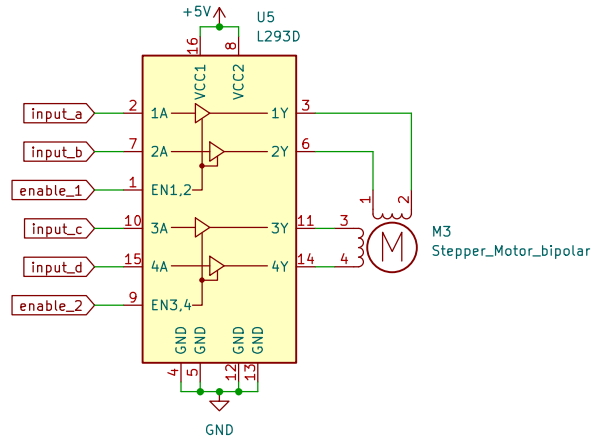Dual H-Bridge Motor Driver  
For driving a stepper motor  
"Forward" "Reverse" "Stop" "OFF"



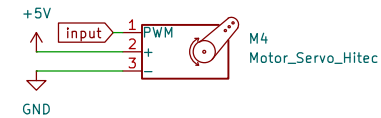Basic Servo Motor (5-6v)  
with typical signal input



5 Ways to implement motors

1 simple servo motor

2x using common L293 motor driver

2x using simple transistor control

**Mason High School Applied Technology**

Sheet: /motors/

File: motors.kicad\_sch

**Title: Motors**

Size: USLetter Date: 2025-04-24

KiCad E.D.A. 8.0.6


**Rev: v1.0**

Id: 6/9


Incandescent Lamp  
(old school lights)



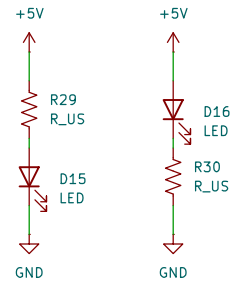Simple LED  
Resistor above  
& below configs




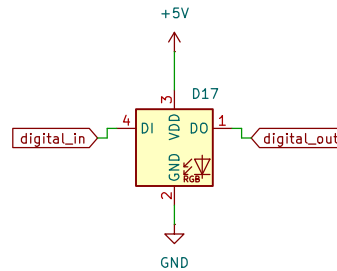Single LED [3528 or 5050 type]  
from an addressable LED strip  
Digital In & Digital Out




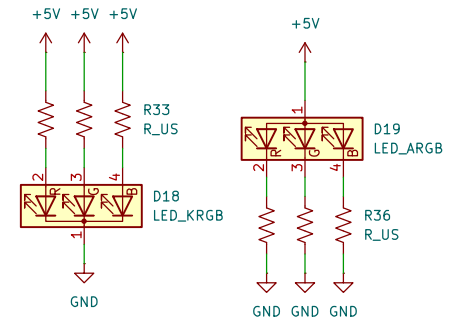**\*\*Especially long or power hungry LED strips will need more elaborate setups: caps, etc.**


3-in-1 RGB LEDs  
common cathode [KRGB] more common  
common anode [ARGB]




CdS Photoresistor  
in voltage divider

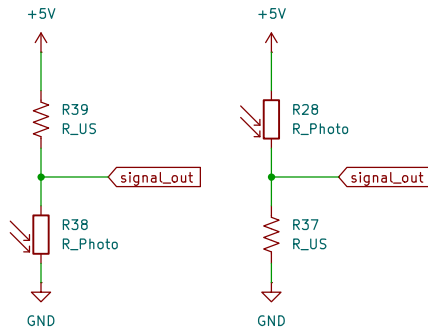

Phototransistor  
in voltage divider

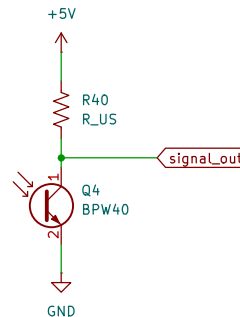

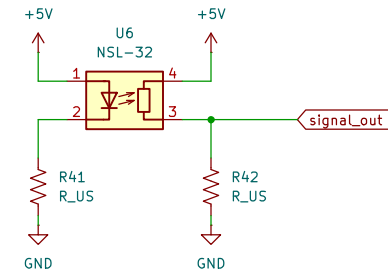Optocoupler  
(link circuits without any  
true electrical connection)



These examples are just the basics:  
Learn about voltage dividers and/or  
transistors—as-switches for added use

4x light outputs that are very common  
3x light inputs (optocoupler is kind of both in/out)  
Various ways to interact with light

**Mason High School Applied Technology**


Sheet: /lights/  
File: lights.kicad\_sch

**Title: Lights**


Size: USLetter Date: 2025-04-24  
KiCad E.D.A. 8.0.6

**Rev: v1.0**  
Id: 7/9


CdS Photoresistor  
in voltage divider

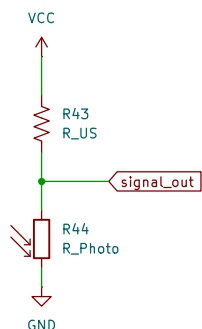


Phototransistor  
in voltage divider

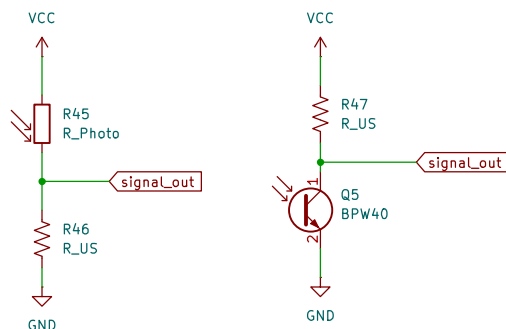



potentiometer  
in voltage divider

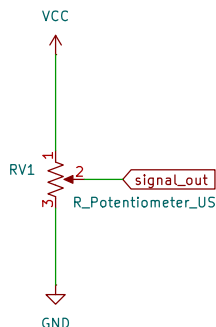

variable resistor  
in voltage divider

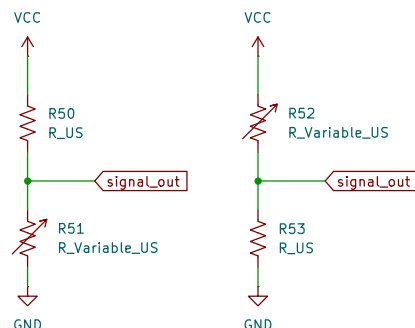


Simple Push-Button  
in voltage divider

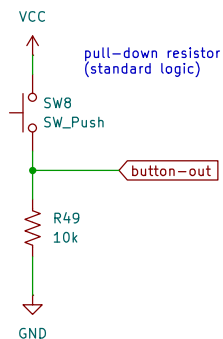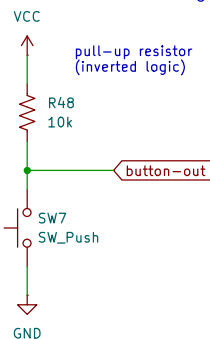

$$V-OUT = VCC \frac{R_b}{R_a + R_b}$$

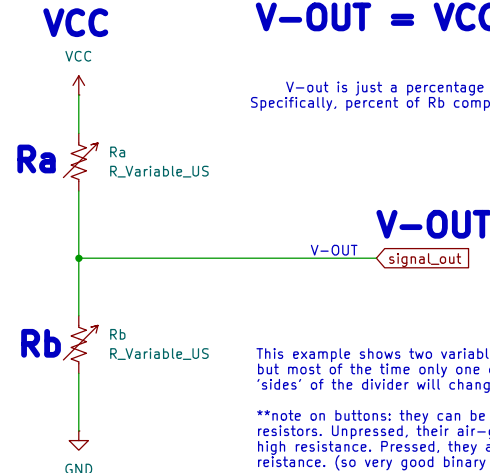V-out is just a percentage of VCC (input).  
Specifically, percent of Rb compared to Ra+Rb total.



This example shows two variable resistors,  
but most of the time only one of the two  
'sides' of the divider will change resistance.

**\*\*note on buttons:** they can be considered as  
resistors. Unpressed, their air-gap is very  
high resistance. Pressed, they are almost-zero  
resistance. (so very good binary voltage dividers)

Voltage dividers use different or changing  
resistance values and 'convert' them into  
changing voltages (for the V-OUT).

This is important, because many circuits,  
microcontrollers, etc. can be controlled  
based on changes in voltage supplied.

Analog inputs (ADCs) can read the V-OUT  
voltages, but you can also use some voltage  
dividers for basic digital signals (if the  
middle-voltages don't cause problems).

So the voltage divider can effectively  
convert quickly electrical properties  
into useful signals and information...

Mason High School Applied Technology

Sheet: /the-voltage-divider/

File: voltage-divider.kicad\_sch

**Title: The Voltage Divider**

Size: USLetter Date: 2025-04-24

KiCad E.D.A. 8.0.6

Rev: v1.0

Id: 8/9